

EDITED BY BILL TRAVIS & ANNE WATSON SWAGER

Two op amps make fast full-wave rectifier

FERNANDO WERLANG, CPQD-TELEBRAS, CAMPINAS, BRAZIL

The circuit in Figure 1 is a precision full-wave rectifier with the following characteristics:

- Minimal delay time between the input and output (with only one op amp in the chain);
- Similar delay times for positive and negative inputs;
- No need to match diodes or adjust resistors.

When $V_{IN} > 0V$, the output of op amp IC_1 is negative, so the reverse-biased diode D_1 blocks the output path of IC_1 to V_{OUT} . The output of op amp IC_2 is positive, so the forward-biased diode D_2 sets the voltage V_B at $V_{IN}(R_6/(R_6+R_5))$. The gain of this noninverting amplifier is $(R_6/(R_6+R_5))(1+R_3/R_4)$.


When $V_{IN} < 0V$, the output of op amp IC_1 is positive, so $V_A = 0V$, diode D_1 becomes forward-biased, and the gain of the inverting amplifier is R_2/R_1 . The output of op amp IC_2 is neg-

ative, so the reverse-biased diode D_2 blocks the output path of IC_2 to V_{OUT} . Three cases are possible for the circuit in Figure 1:

- For unity gain, $R_3=R_5=0\Omega$, $R_4=R_6=\infty$, and $R_1=R_2$. For the project that led to this design, $R_1=R_2=4.75k\pm 1\%$, and the input is a sine wave at 25 Hz and 4V rms.
- For gains greater than unity, $R_5=0\Omega$, $R_6=\infty$, and the gain is $R_2/R_1=(1+R_3/R_4)$. Satisfying this gain equation yields equal gains for positive and negative input signals.
- For gains lower than unity, $R_3=0\Omega$, $R_4=\infty$, and the gain is $R_2/R_1=R_6/(R_6+R_5)$. Satisfying this gain equation yields equal gains for positive and negative input signals. (DI #1837)

EDN

To Vote For This Design, Circle No. 359

 

You can obtain precision full-wave rectification with any desired gain, with no need to match diodes or trim resistors.

Network forms digital-to-impedance converter

ALEX BELOUSOV, SMP INC, REGO PARK, NY

Circuit in Figure 1 resembles a capacitive-ladder (C-2C) I/V converter. However, it does not provide conversion from a digital code to a voltage or current, but rather converts the digital code to a capacitor value. The C-2C topology is well-suited for IC or hybrid implementation, as it calls

for only two nominal values. You can prove mathematically that the equivalent capacitance between terminals 1 and 2 is $C_{EQ}=2C \cdot (D_i \cdot 2^{-i})$, where D_i represents the binary coefficients of the digital-input code.

The follower IC_1 keeps both buses I_1 and I_2 at equal poten-